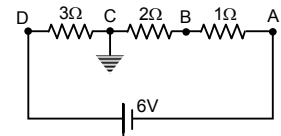


CONTINUED FROM SAKSHI VIDYA (09.01.2010)  
CURRENT ELECTRICITY


11. For the circuit shown in figure, the potentials of point A, B, C and D are  $V_A$ ,  $V_B$ ,  $V_C$  and  $V_D$  respectively. Then

- 1)  $V_A = 1V$ ,  $V_B = 2V$ ,  $V_C = 0V$ ,  $V_D = -2V$
- 2)  $V_A = 3V$ ,  $V_B = -2V$ ,  $V_C = 0V$ ,  $V_D = 3V$
- 3)  $V_A = -3V$ ,  $V_B = -2V$ ,  $V_C = 0V$ ,  $V_D = 3V$
- 4)  $V_A = 3V$ ,  $V_B = 2V$ ,  $V_C = 0V$ ,  $V_D = -3V$




12. The equivalent resistance between points A and B of the circuit given below is

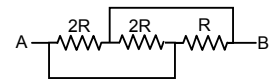- 1) R
- 2)  $R/2$
- 3)  $2R$
- 4)  $R/3$




13. In the circuit shown in figure the heat produced in the  $5\Omega$  resistor due to the current flowing through it is 10 calories per second. The heat generated in the  $4\Omega$  resistor is

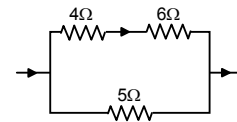- 1) 1 cal/s
- 2) 2 cal/s
- 3) 3 cal/s
- 4) 4 cal/s



14. A battery of internal resistance  $4\Omega$  is connected to the network of resistances as shown. In order that the maximum power can be delivered to the network, the value of R in  $\Omega$  should be

- 1)  $4/9$
- 2) 2
- 3)  $8/3$
- 4) 18

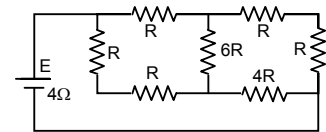

15. A steady current flows in a metallic conductor of non-uniform cross-section. The quantity/quantities constant along the length of the conductor is/are


- 1) current, electric field and drift speed
- 2) drift speed only
- 3) current and drift speed
- 4) current only

16. A wire of length L and 3 identical cells of negligible internal resistances are connected in series. Due to the current, the temperature of the wire is raised by  $\Delta T$  in a time t. A number N of similar cells is now connected in series with a wire of the same material and cross-section but of length 2L. The temperature of the wire is raised by the same amount  $\Delta T$  in the same time. The value of N is

- 1) 4
- 2) 6
- 3) 8
- 4) 9


17. In the given circuit, with steady current, the potential drop across the capacitor must be

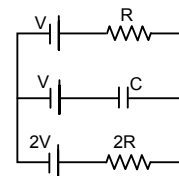- 1) V
- 2)  $V/2$
- 3)  $V/3$
- 4)  $2V/3$




18. The effective resistance between points P and Q of the electric circuit shown in the figure is

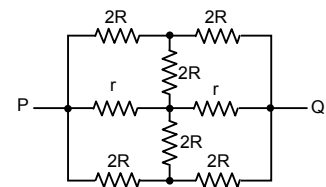- 1)  $\frac{2Rr}{R+r}$
- 2)  $\frac{8R(R+r)}{3R+r}$
- 3)  $2r + 4R$
- 4)  $\frac{5R}{2} + 2r$



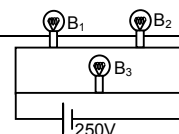19. A 100 W bulb  $B_1$ , and two 60 W bulbs  $B_2$  and  $B_3$ , are connected to a 250 V source, as shown




in the figure. Now  $W_1$ ,  $W_2$  and  $W_3$  are the output powers of the bulbs  $B_1$ ,  $B_2$  and  $B_3$  respectively. Then

- 1)  $W_1 > W_2 = W_3$
- 2)  $W_1 > W_2 > W_3$
- 3)  $W_1 < W_2 = W_3$
- 4)  $W_1 < W_2 < W_3$

20. In the shown arrangement of the experiment of the meter bridge if AC corresponding to null deflection of galvanometer is  $x$ , what would be its value if the radius of the wire AB is doubled?

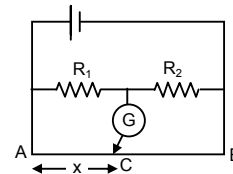- 1)  $x$
- 2)  $x/4$
- 3)  $4x$
- 4)  $2x$



**Key :**

11) 3, 12) 2, 13) 2, 14) 2, 15) 4, 16) 2, 17) 3, 18) 1, 19) 4, 20) 1