
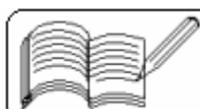


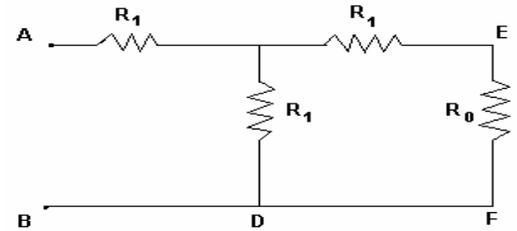- 1) Resistance of silver wire is  $3 \Omega$  at  $30^\circ \text{C}$  and at  $100^\circ \text{C}$ , it is  $3.5 \Omega$ . Find its temperature coefficient of resistance. [ March, 2003 ]  
( Ans:  $2.44 \times 10^{-3} \text{ }^\circ\text{C}^{-1}$  )
- 2) Resistance of a wire is  $10.5 \Omega$  at  $21^\circ \text{C}$  and at  $147^\circ \text{C}$  it is  $16.5 \Omega$ . Find its temperature coefficient of resistance. [ April, 2002 ]  
( Ans:  $4.56 \times 10^{-3} \text{ }^\circ\text{C}^{-1}$  )
- 3) A conducting wire has a resistance of  $20 \text{ ohm}$ . Its length is now stretched to increase by  $2\%$ . Calculate the resulting value of the resistance of the wire. [ March, 2002 ]  
( Ans:  $20.8 \Omega$  )
- 4)  $5 \text{ metre}$  long wire is connected with cell. The e. m. f. and internal resistance of the cell are  $2.5 \text{ V}$  and  $0.5 \Omega$ . The resistance of wire is  $2 \Omega$ . Find the potential gradient on the wire. [ October, 1998 ]  
( Ans:  $0.4 \text{ V/m}$  )
- 5) Two resistors  $15 \Omega$  and  $B \Omega$  are connected in parallel. This combination is connected in series to a  $5 \Omega$  resistor and a battery of e. m. f.  $5 \text{ volt}$ . If the current through  $B \text{ ohm}$  resistor is  $1/3 \text{ A}$ , find the value of  $B$ . [ March, 1998 ]  
( Ans:  $7.5 \Omega$  )
- 6) A pyramid is constructed from six conductive wires each of resistance 'R'. Calculate the effective resistance between any two vertices of the pyramid. [ October, 1997, October, 1996 ]  
( Ans:  $R/2$  )
- 7) Three batteries  $E_1 = 1.5 \text{ V}$ ,  $E_2 = 2.5 \text{ V}$  and  $E_3 = 3.5 \text{ V}$  and a resistance  $R = 10 \Omega$  are connected in series to make a loop of closed circuit. In this  $E_2$  and  $E_3$  are in helping position and  $E_1$  is in opposite position. Now  $5 \Omega$  resistance is connected in parallel to  $E_2$ . Find the current passing through  $10 \Omega$  and  $5 \Omega$  resistance and battery  $E_2$ . [ March, 1997 ]  
( Ans:  $0.45 \text{ A}$ ,  $0.5 \text{ A}$  and  $0.95 \text{ A}$  )
- 8) An electron of mass  $9 \times 10^{-28} \text{ gm}$  and charge of  $1.6 \times 10^{-19} \text{ C}$  moves in a conductor with acceleration of  $10^{12} \text{ m/s}^2$ . Find potential gradient of the conductor. [ March, 1996 ]  
( Ans:  $5.625 \text{ V/m}$  )
- 9) Unknown resistance  $X$  is joined parallel to a resistance of  $20 \Omega$ . To this combination a battery of  $2 \text{ volt}$  and resistance of  $10 \Omega$  are joined in series. If the current passing through  $X$  is  $0.05 \text{ amp}$ , find the value of  $X$ . [ March, 1992 ]  
( Ans:  $20 \Omega$  )
- 10) A cell of e. m. f  $1.5 \text{ volts}$  is connected in parallel with two resistances of  $5 \Omega$  and  $12 \Omega$ . Determine the current flowing from the cell as well as the current flowing through the two resistances. [ March, 1987 ]  
( Ans:  $0.425 \text{ A}$ ,  $0.3 \text{ A}$ ,  $0.125 \text{ A}$  )



- 11) The resistances of the four arms AB, BC, CD and DA of a balanced Wheatstone bridge are respectively 10, 20, 30 and x ohms. Find the value of the unknown resistance x.  
( Ans: 15  $\Omega$  ) [ May, 1986 ]

- 12) Find input resistance  $R_{AB}$  between points A and B in forms of  $R_0$  and  $R_1$  in the adjoining circuit.  
[ October, 1990 ]




[ Ans:  $R_1 + R_1(R_1 + R_0) / (2R_1 + R_0)$  ]

- 13) Find the resistance of a copper wire 30 m long and 1 mm in diameter. Resistivity of copper =  $1.7 \times 10^{-6}$  ohm-cm.  
( Ans: 0.65  $\Omega$  )
- 14) The resistance of a wire 2.5 m long and 0.9 mm in diameter is 0.07 ohm. What is the resistivity of the material of the wire ?  
( Ans:  $1.8 \times 10^{-6}$  ohm-cm )
- 15) The resistance of a coil of copper wire is 5  $\Omega$  at 25° C. Determine its resistance at 0° C and 100° C. Temperature coefficient of resistivity of copper =  $4.3 \times 10^{-3} / ^\circ\text{C}$  ( $\alpha_{20}$ ).  
( Ans: 4.47  $\Omega$ , 6.58  $\Omega$  )
- 16) A standard resistance coil marked 5  $\Omega$  is found to have a resistance of 5.2  $\Omega$  at 40° C. Find the temperature at which the marking is correct. Temperature coefficient of resistivity of the material of the wire = 0.005 per °C ( $\alpha_{20}$ ).  
( Ans: 31.5° C )
- 17) Calculate the loss in watts per kg of a current carrying conductor in terms of the resistivity  $\rho$   $\mu\Omega$  - cm, the current density  $\sigma$  amp / mm<sup>2</sup> and specific gravity S.  
( Ans:  $10 \sigma^2 \rho / S$  )
- 18) A copper and an iron conductor are connected in parallel. If the same current flows through each at 0° C, what proportion of current will flow through each at 100° C ? Temperature coefficient of resistivity of copper and iron are 0.0043 and 0.0063 per °C .  
( Ans: 53.9 % through copper wire and 46.1 % through iron wire )
- 19) What equal lengths of iron wire and a constantan wire, each of 1 mm diameter must be joined in parallel to give an equivalent resistance of 2 ohm ? Resistivities of iron and constantan are 10 and 49 microohm-cm respectively. ( Ans: 18.9 m )
- 20) Calculate the specific resistance of the material of a wire 24 cm in length, 0.003 cm in diameter and having a resistance of 162 ohm. Also find to what length the wire must be drawn to give it a resistance of 288 ohm. Assume that no change in specific resistance and density occurs in such process.  
( Ans:  $4.77 \times 10^{-5}$  ohm-cm, 32 cm )
- 21) Determine the length l and diameter d of a cylinder of copper in terms of the volume x, resistivity  $\rho$  and the resistance between opposite ends, r.  
( Ans:  $l = (rx / \rho)^{1/2}$ ,  $d = (16x\rho / \pi^2 r)^{1/4}$  )


- 22) Resistances of  $60\ \Omega$  and  $40\ \Omega$  are connected in series with a  $9\ \text{V}$  battery. A voltmeter connected in parallel with  $60\ \Omega$  resistance shows  $4.5\ \text{V}$ . (1) Find the resistance of the voltmeter. (2) What will be the deflection in the voltmeter if it is connected in parallel with  $40\ \Omega$  resistance? (3) What will be the potential difference across the  $40\ \Omega$  resistance if no voltmeter is connected? (4) How much less will the voltmeter show from the true value?  
 (Ans: (1)  $120\ \Omega$ , (2)  $3\ \text{V}$ , (3)  $3.6\ \text{V}$ , (4)  $0.6\ \text{V}$ )

- 23) When two resistors are connected in series, their equivalent resistance is  $18\ \Omega$  and when they are connected in parallel, the equivalent resistance is  $4\ \Omega$ . Find their resistances. (Ans:  $12\ \Omega$ ,  $6\ \Omega$ )

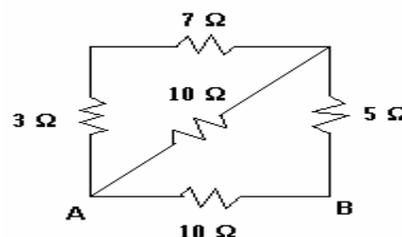- 24) Five resistances are connected as shown in the diagram. Find the equivalent resistance between the points A and B.  
 (Ans:  $5\ \Omega$ )




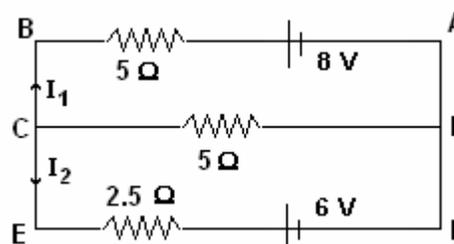- 25) Determine the current through each branch in the adjoining circuit.  
 (Ans:  $I_1 = 0.6\ \text{A}$ ,  $I_2 = 0.4\ \text{A}$ )



- 26) A resistance is made by joining two wires of the same material. The radii of the two wires are  $1\ \text{mm}$  and  $3\ \text{mm}$  respectively, while their lengths are  $3\ \text{cm}$  and  $5\ \text{cm}$  respectively. A battery of emf  $16\ \text{V}$  and negligible internal resistance is connected across the resistance. What is the potential drop along the shorter wire?  
 (Ans:  $13.5\ \text{V}$ )

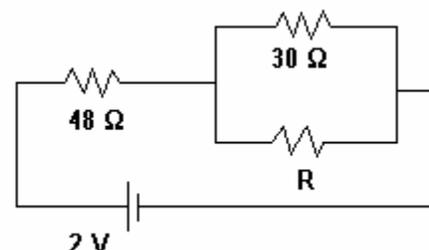- 27) In the circuit shown, when  $R$  is removed, additional resistance of  $72\ \text{ohm}$  must be inserted in series with the battery in order to keep the current in the  $30\ \text{ohm}$  resistor unaltered. Find the value of  $R$ .  
 (Ans:  $20\ \Omega$ )



- 28) Two resistances,  $60\ \Omega$  and  $80\ \Omega$  are connected in series with a dynamo supplying an emf of  $34\ \text{V}$ . When a voltmeter of resistance  $R\ \Omega$  is connected across the  $80\ \Omega$  resistance, it reads  $16\ \text{V}$ . (a) Calculate the resistance of the voltmeter. (b) If this voltmeter is connected across  $60\ \Omega$  resistance, what will be its reading?  
 (Ans: (a)  $160\ \Omega$ , (b)  $12\ \text{V}$ )

- 29) 24 identical cells each of emf  $2\ \text{V}$  and internal resistance  $2\ \text{ohm}$  are arranged to send current through an external resistance of  $3\ \text{ohm}$ . Find the best arrangement of cells. Find also the maximum current through the external resistance.  
 (Ans: 4 rows with 6 cells in a row;  $2\ \text{ampere}$ )